
## November 24, 2023

## question

- 1. In the cricult shift, the initial binary content of the shift register A 1101 and that of shift register B is 1010 The shift registers are positive edge triggered, and the gates have no delay.
  - when the shift control is high, what will be the binary content of the shift registers A and B after clock pulses ?

GATE IN 2023

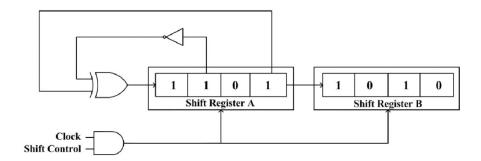

- (a) A = 1101, B = 1101
- (b) A = 1110, B = 1001
- (c) A = 0101, B = 1101
- (d) A = 1010, B = 1111