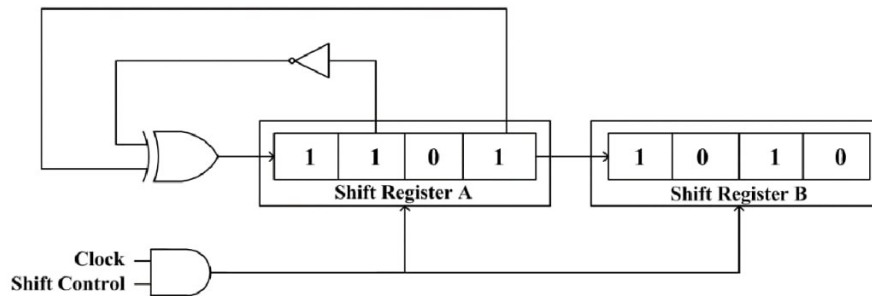


November 22, 2023

question

1. In the cricult shift, the initial binary content of the shift register A 1101 and that of shift register B is 1010 The shift registers are positive edge triggered, and the gates have no delay.

when the shift control is high, what will be the binary content of the shift registers A and B after clock pulses ?



- (a) $A = 1101, B = 1101$
- (b) $A = 1110, B = 1001$
- (c) $A = 0101, B = 1101$
- (d) $A = 1010, B = 1111$